

ASSIGNMENT #2

(Dr. Waseem Ikram)

ID #BC210402929


(Muhammad Umair)

Question #1

You are given a customized PLA based device (programming AND & programmable XOR arrays) having 10 inputs and 3 outputs.

You are required to perform the stated operations:

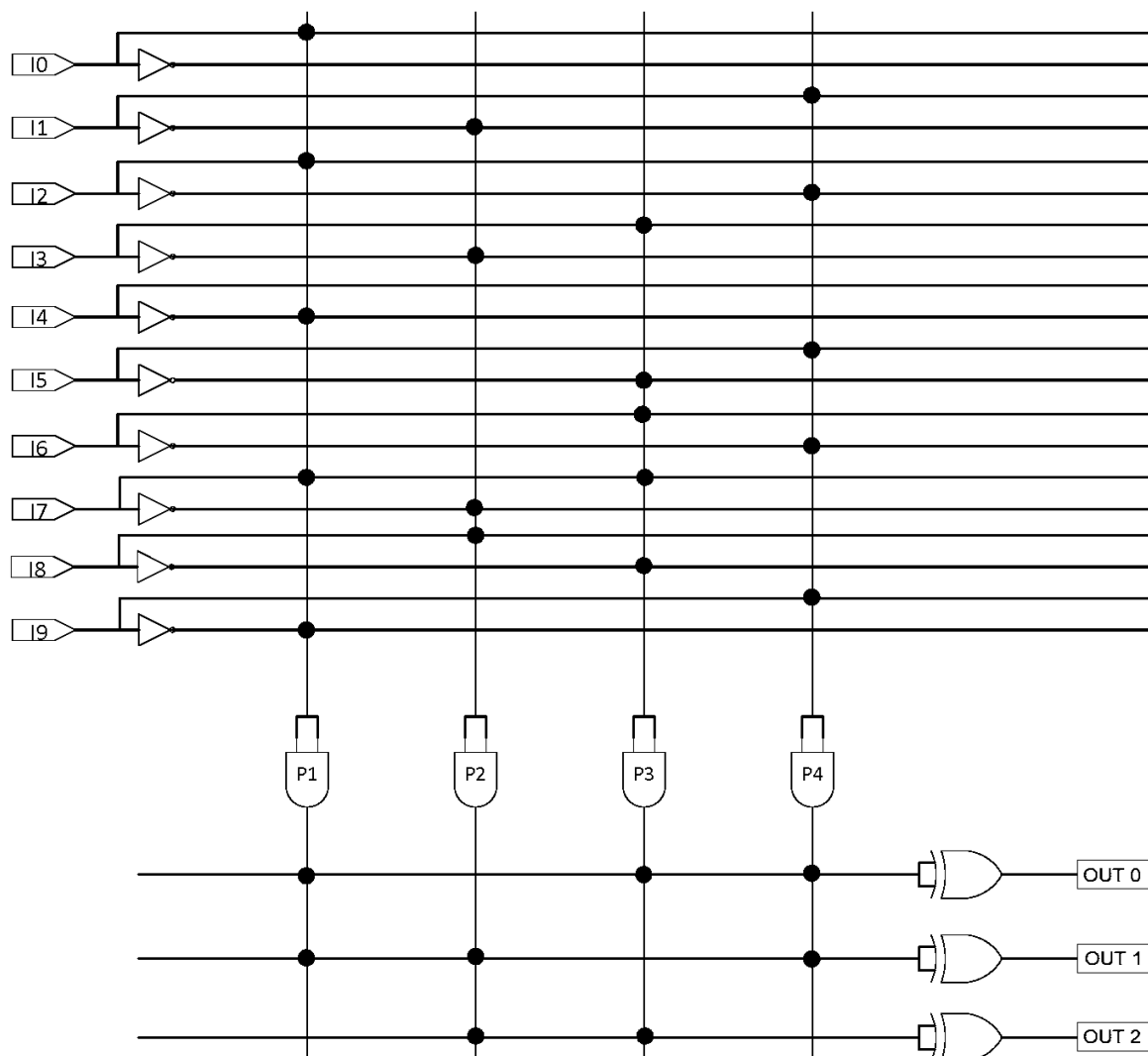- Generate the basic Boolean Expression of the stated circuit.
- Convert the generated Boolean Expression into ABEL Expression.



Solution

First we generate the basic Boolean Expression of the stated circuit,

Points	I	II	III	IV	V
P1	i0	i2	i4'	i7	i9'
P2	i1'	i3'	i7'	i8	
P3	i3	i5'	i6	i7	i8'
P4	i1	i2'	i5	i6'	i9

We get the following generated product terms,

$$P1 = i0.i2.i4'.i7.i9'$$

$$P2 = i1'.i3'.i7'.i8$$

$$P3 = i3.i5'.i6.i7.i8'$$

$$P4 = i1.i2'.i5.i6'.i9$$

For given OUTPUT are:

$$O1 = P1 \oplus P3 \oplus P4$$

$$O2 = P1 \oplus P2 \oplus P4$$

$$O3 = P2 \oplus P3$$

By putting the values of product terms in OUTPUT,

$$O1 = i0.i2.i4'.i7.i9' \oplus i3.i5'.i6.i7.i8' \oplus i1.i2'.i5.i6'.i9$$

$$O2 = i0.i2.i4'.i7.i9' \oplus i1'.i3'.i7'.i8 \oplus i1.i2'.i5.i6'.i9$$

$$O3 = i1'.i3'.i7'.i8 \oplus i3.i5'.i6.i7.i8'$$

Now, converting the generated Boolean Expression into ABEL Expression,

$$O1 = i0 \&i2 \&!i4 \&i7 \&i9 \$ i3 \&i5 \&i6 \&i7 \&!i8 \$ i1 \&!i2 \&i5 \&!i6 \&i9$$

$$O2 = i0 \&i2 \&!i4 \&i7 \&i9 \$!i1 \&!i3 \&!i7 \&i8 \$ i1 \&!i2 \&i5 \&!i6 \&i9$$

$$O3 = !i1 \&!i3 \&!i7 \&i8 \$ i3 \&!i5 \&i6 \&i7 \&!i8$$