

ASSIGNMENT #1

(Dr. Waseem Ikram)

ID #BC210402929

(Muhammad Umair)

Question #1

You are required to draw the NAND based Circuit Diagram for the given boolean expressing using Electronic WorkBench (Logic Converter).


$$Z = AB(\bar{C} + \bar{D}) + \bar{E}\bar{F} + \bar{A}F + \bar{A}E(\bar{B} + F) + EF + CD(\bar{A} + \bar{E}) + \bar{A}\bar{F}$$

Solution

Given Expression

$$AB(C'+D')+E'F'+A'F+A'E(B'+F)+EF+CD(A'+E')+A'F'$$

Screenshot

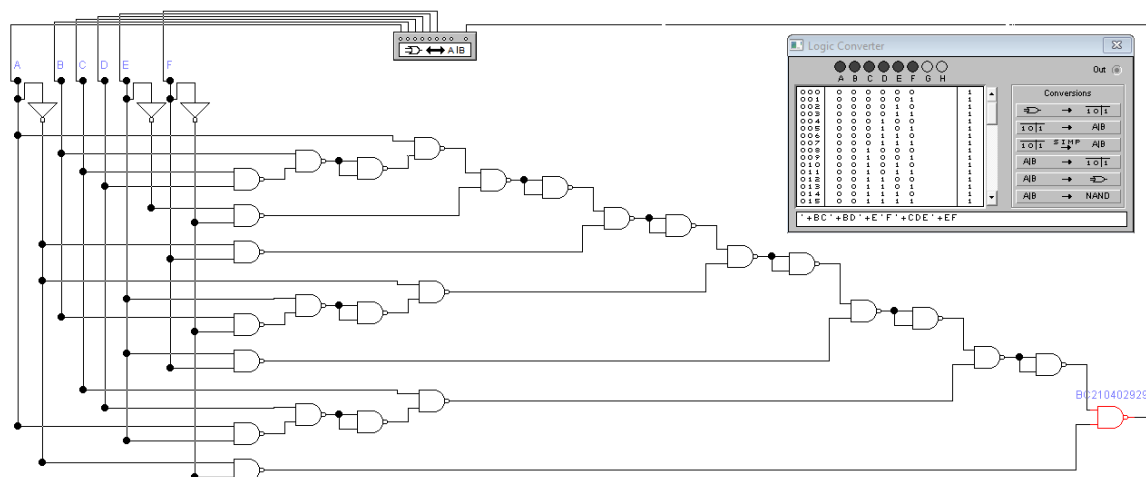

Simplified Expression

$$A'+BC'+BD'+E'F'+CDE'+EF$$